

NAME: ANKIT GUHA

ROLL: 200108062

EXAM: ENDSEM

COURSE: EE210

DATE: 25/11/21

⑧ BCD to 7 segment decoder requires 5 inputs and 7 outputs.

4 inputs specify 32 ( $2^5$ ). So the ROM size must be  $32 \times 7$ .

4-bit adder sub:

Inputs								Output					Decimal
$A_3$	$A_2$	$A_1$	$A_0$	$B_3$	$B_2$	$B_1$	$B_0$	$C_4$	$C_3$	$C_2$	$C_1$	$C_0$	
0	0	0	0	0	0	0	0	0	0	0	0	0	0
-	-	-	-	-	-	-	-	-	-	-	-	-	-
0	1	1	1	1	1	1	1	1	1	1	1	0	30
1	0	0	0	0	0	0	0	0	0	0	0	0	0
-	-	-	-	-	-	-	-	-	-	-	-	-	-
1	1	1	1	1	1	1	1	0	0	0	0	0	0

where selection input  $S = 0$   
 $2 \times 7 = 512 \times 5$   
 $\left\{ \begin{array}{l} 9 \text{ inputs} \\ 5 \text{ outputs} \end{array} \right\}$   
 $= 512 (2^9)$

$$\begin{aligned} \textcircled{*} \quad (24)_5 &= (2 \times 5^1 + 4 \times 5^0)_{10} \\ &= (10 + 4)_{10} \\ &= (14)_{10} \\ &= (010100)_{BCP} \end{aligned}$$

$$(10010011001)_{BC5} = (100 \ 010 \ 011 \ 001)_{BC4} = (4231)_5$$

$\textcircled{*}$  In always block, the clk signal will remain 0 for  $(x+3)$  time units and will remain 1 for 4 time units in loop.

Duty cycle will be given by  $\frac{4}{x+7}$

$$\begin{aligned} \text{Solving, } \frac{4}{x+7} &= 0.25 \\ \Rightarrow x &= 9 \end{aligned}$$

$\textcircled{*}$  Frequency of clk =  $f$ .  
Here, T-flip flop acts as frequency divider. Frequency of  $Q = \frac{f}{2}$ .

$$Y = \text{clk} \oplus Q$$

$$\text{Freq of } Y = \frac{f}{2}$$



- ① In the given circuit, the 3 bit counter converts the given decimal into gray code.

The output of gray code is connected to the selection lines of multiplexer.


The output of multiplexer is pulled low. Therefore the output is 0 when multiplexer is not enabled.

Decimal	Binary	Gray code	S <sub>2</sub> S <sub>1</sub> S <sub>0</sub> E	Output
0	000	000	000	I <sub>0</sub>
1	001	001	001	0
2	010	011	011	0
3	011	010	010	I <sub>1</sub>
4	100	110	110	I <sub>3</sub>
5	101	111	111	0
6	110	101	101	0
7	111	100	100	I <sub>2</sub>

- ② Pass transistor logic

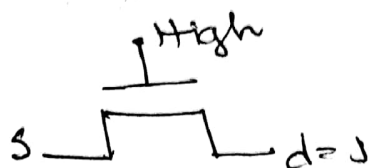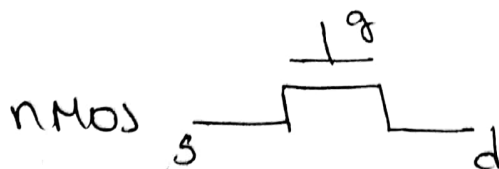


$$\text{if } g=0 \Rightarrow d=\bar{s}$$

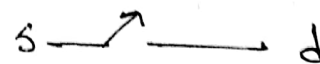

$$\text{if } g=1 \Rightarrow d=s$$



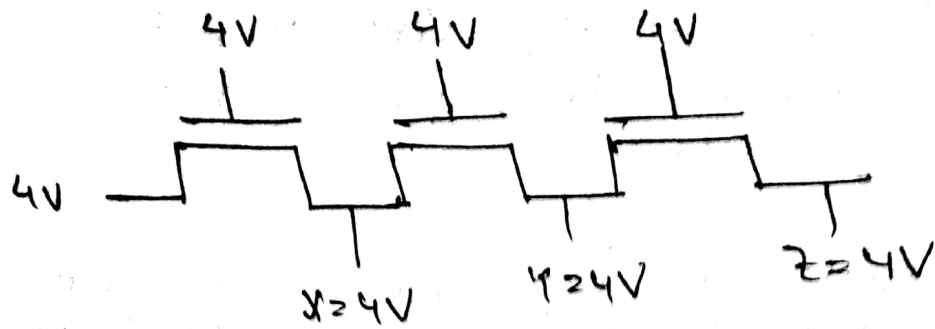

$$x = 4V$$

$$y = 4V$$

$$z = 4V$$

⊛ Since it is non-blocking assignment,

$$d = 5 + 17 \\ = 22$$

⊛ From the code

if  $b = 00 \Rightarrow a = 0;$

if  $b = 11 \Rightarrow a = 0;$

if  $b$  is other than 00s 11  
 $\Rightarrow a = 1$

Truth table:

$b[1]$	$b[0]$	$a$
0	0	0
0	1	1
1	0	1
1	1	0

$$\Rightarrow a = b[1] \oplus b[0]$$

Ankit Gulay 200108062

A combination circuit implementing a XOR function will be generated.

From circuit diagram,

$$Y = AX_1 + \bar{A}X_0$$

$$X_1 = Q, X_0 = \bar{Q}$$

$$\Rightarrow Y = AQ + \bar{A}\bar{Q}$$

Excitation table of D-flip-flop is

$$Q(t+1) = D$$

$$\Rightarrow Q(t+1) = Y$$

$$\Rightarrow Q(t+1) = AQ + \bar{A}\bar{Q}$$

if  $Q = 0$ ,

$$Q(t+1) = \bar{A} + 0 \\ = \bar{A}$$

if  $A = 0$ ,

$$Q(t+1) = 1 \Rightarrow A = Y = 0$$

if  $A = 1$ ,

$$Q(t+1) = 0 \Rightarrow A = Q = 1$$

if  $Q = 1$ ,

$$Q(t+1) = 0 + A \\ = A$$

if  $A = 0$ ,

$$Q(t+1) = 0 \Rightarrow A = Q = 0$$

if  $A = 1$ ,

$$Q(t+1) = 1 \Rightarrow A = Q = 1$$

$$X = 0, Y = 0, W = 1, Z = 1$$

Ankit Guha, 200108062.

\* Given  $F(A,B,C,D) = \pi(1,5,12,15)$   
in terms of minterms.

$$F(A,B,C,D) = \Sigma(0,2,3,4,6,7,8,9,10,11,13,14)$$

Truth table:-

A	B	C	D	minterms	F
0	0	0	0	0	1
0	0	0	1	1	0 $F=0$
0	0	1	0	2	1
0	0	1	1	3	1 $F=1$
0	1	0	0	4	1
0	1	0	1	5	0 $F=0$
0	1	1	0	6	1
0	1	1	1	7	1 $F=1$
1	0	0	0	8	1
1	0	0	1	9	1 $F=1$
1	0	1	0	10	1
1	0	1	1	11	1 $F=1$
1	1	0	0	12	0
1	1	0	1	13	1 $F=1$
1	1	1	0	14	1
1	1	1	1	15	0 $F=0$

$$* \textcircled{1} \quad X = \overline{(0 \oplus 0)} \overline{(0 \oplus 0)}$$

we know  $0 \oplus 0 = 1 \therefore \overline{0 \oplus 0} = 0$   
 $\Rightarrow X = 1$  always

If input = 1 always, then output will be changed only at ~~positive~~ negative edge of clock.

$$\boxed{f_1 = f_2 = 0.5 \text{ kHz}}$$

\* \textcircled{2}

$$V_x = \text{SOP}$$

$$= \overline{P_1 + P_2}$$

$$= \overline{AC + BC} = \overline{(A+B)C}$$

$$V_o = \overline{\text{SOP}}$$

$$= \overline{P_1}$$

$$= \overline{V_x} = \overline{\overline{(A+B)C}} = (A+B)C$$

{ no. of product terms = no. of parallel paths from o/p to GND

literals present in pat term = 1/p of those bi, which present in that path.



Ankit Gupta 200108062

$$\textcircled{*} V_{OL} = (V_{DD} - V_t) \left[ 1 - \sqrt{1 - \frac{1}{8}} \right] = (2.5 - 0.5) \left[ 1 - \sqrt{1 - \frac{1}{8}} \right] \\ = 2 \left[ 1 - \sqrt{\frac{3}{8}} \right] = 0.268$$

$$V_{IL} = V_t + \frac{V_{DD} - V_t}{\sqrt{4(8+1)}} = 0.5 + \frac{2.5 - 0.5}{\sqrt{4 \times 5}} \\ = 0.947$$

$$V_H = V_t + \frac{V_{DD} - V_t}{\sqrt{4+1}} = 0.5 + \frac{2}{\sqrt{5}} = 1.394$$

$$V_{IH} = V_t + \frac{2}{\sqrt{3 \times 4}} (V_{DD} - V_t) = 0.5 + \frac{2}{\sqrt{12}} (2) \\ = 1.654$$

$$V_{OH} = V_{DD} = 2.5V$$

$$NM_L = V_{IL} - V_{OL} = 0.679$$

$$NM_H = V_{OH} - V_{IH} = 0.846$$

$$\textcircled{*} \quad \left(\frac{\omega}{L}\right)_n = \frac{0.325}{0.18}$$

$$r = \gamma = \frac{40 \times 0.325 / 0.18}{120 \times \left(\frac{\omega}{L}\right)_p}$$

$$\left(\frac{\omega}{L}\right)_p = 1.35$$

$$k_p' = k_p \left(\frac{\omega}{L}\right)_p = 54$$

$$\begin{aligned} \therefore I_{\text{stat}} &= \frac{1}{2} k_p' (V_{DD} - V_t)^2 = \frac{1}{2} \times 54 \times 4 \\ &= 108 \mu\text{A} \\ &= 0.108 \text{ mA} \end{aligned}$$

$$\begin{aligned} D_p &= (0.108) V_{DD} = 0.108 \times 2.5 \\ &= 0.270 \text{ mW} \end{aligned}$$

$\textcircled{*}$  At time  $= t_1$   
 $\omega = 0110$   
 $A = 0110$  at pos edge

The address will be 6.

$\therefore \omega = 1010$   
 $A = 1010$  at pos edge

↓  
 Address  $= 10$

$\therefore \omega = 1000$  at time  $t_2$ .